
 


Lab Session 2 – Festo MecLab Logic

 
Basic logic elements: - Please complete the logic tables to the given logic circuits




I1	I2	I3	I4	I5	I6	Q1	Q2	Q3	Q4



I1	I2	I3	I4	I5	I6	Q1	Q2	Q3	Q4

 


I1	I2	I3	I4	I5	I6	Q1	Q2	Q3	Q4

 

I1	I2	I3	I4	I5	I6	Q1	Q2	Q3	Q4

RS-FlipFlops

 

I1	I2	I3	I4	I5	I6	Q1	Q2	Q3	Q4

Complete the following timing diagram:

